

Bipolar (npn) Transistor Exercises

Question 1

Draw the circuit symbol for an npn Bipolar Transistor

Label the connections with the correct names

Question 2

Describe the action of an npn Bipolar Transistor (when used as a transducer driver) in terms of current and voltage

Question 3

Write down the equation connecting current and transistor gain


Explain what each of the terms in the equation represent

Question 4

A Bipolar Transistor is used to control a 24 W lamp from a 12 V supply. The push button is connected to the same 12 V supply.

The gain of the transistor is $\times 100$.

Calculate the value of the base resistor, R_B

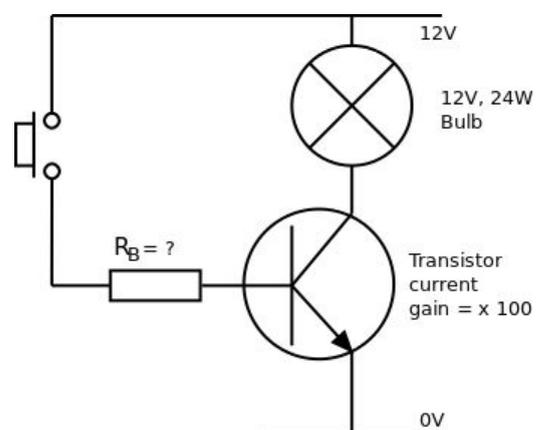

Question 5

A logic circuit is used to control a motor using an npn Bipolar Transistor. The logic circuit has an output of 5 V and can supply a maximum current of 20 mA. The motor works from a 24 V supply and requires a maximum current of 1.5 A

- What is the minimum current gain of the transistor?
- As well as the base resistor, what additional component is needed?
- Calculate a suitable value for the base resistor for this circuit


Bipolar (npn) Transistor Answers

Question 1

c = Collector

e = Emitter

b = Base

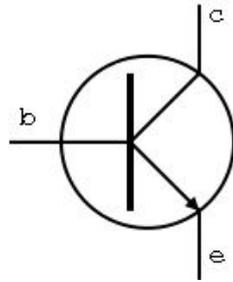

Question 2

When the potential difference (voltage) between the Base and the Emitter is less than 0.7V the transistor is “off” and no current flows from the Collector to the Emitter. When the potential difference between the Base and Emitter is 0.7V the transistor is “on” and current flows into the Base allowing current to flow from the Collector to the Emitter.

Question 3

$$I_C = h_{FE} \times I_B$$

I_C = Collector current

I_B = Base current

h_{FE} = Current gain

Question 4

- Using $I = P/V$, the current in the bulb is $24/12 = 2\text{ A}$
- Therefore the Collector current is $I_C = 2\text{ A}$
- Using $I_B = I_C / h_{FE}$, the Base current is $2/100$ giving $I_B = 0.02\text{ A}$
- The voltage drop across the Base resistor is $12 - 0.7 = 11.3\text{ V}$
- Using $R = V/I$, the Base resistor is $R_B = 11.3 / 0.02 = 565\ \Omega$. Use $R_B = 560\ \Omega$

Question 5

- a) $h_{FE} = I_C / I_B = 1.5 / 0.02 = 75$ (minimum)
- b) A diode reverse biased across the motor to protect the transistor
- c) $R_B = (5 - 0.7) / 0.02 = 215\ \Omega$