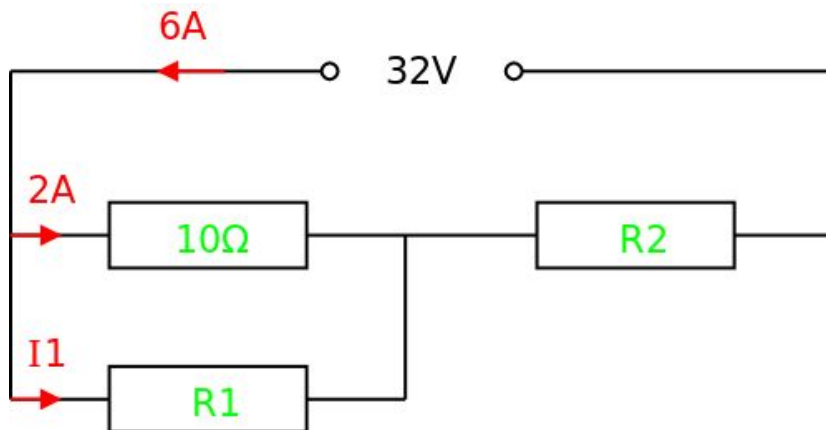


Resistance Questions

The diagram shows a power supply connected to a simple circuit made from three resistors.



Use the information on the circuit diagram to answer questions 1 to 7 below.

Question 1

What is the potential difference across the $10\ \Omega$ resistor?

- A: 32 V
- B: 20 V
- C: 16 V
- D: 5 V

Question 2

What is the current I_1 flowing into resistor R_1 ?

- A: 6 A
- B: 4 A
- C: 3 A
- D: 2 A

Question 3

What is the potential difference across resistor R_1 ?

- A: 20 V
- B: 16 V
- C: 8 V
- D: 4 V

Question 4

What is the value of resistor R1?

- A: 20 Ω
- B: 10 Ω
- C: 5 Ω
- D: 4 Ω

Question 5

What is the potential difference across resistor R2?

- A: 32 V
- B: 20 V
- C: 16 V
- D: 12 V

Question 6

What is the current flowing through resistor R2?

- A: 6 A
- B: 4 A
- C: 3 A
- D: 2 A

Question 7

What is the value of resistor R2?

- A: 10 Ω
- B: 5 Ω
- C: 3 Ω
- D: 2 Ω

Question 8

A potential difference of 9 V causes a current of 0.2 mA to flow in a resistor. What is the value of the resistor?

- A: 45 k Ω
- B: 18 k Ω
- C: 45 Ω
- D: 18 Ω

Question 9

There is a potential difference of 0.5 V across a 500 Ω resistor. What current flows through the resistor?

- A: 1 A
- B: 0.1 A
- C: 0.01 A
- D: 0.001 A

question 10

A current of 20 mA flows through a 4.7 k Ω resistor. What is the applied potential difference?

- A: 94,000 V
- B: 94 V
- C: 0.24 V
- D: 0.094 V

Answers

1. B
2. B
3. A
4. C
5. D
6. A
7. D
8. A
9. D
10. B

Website

http://www.pfnicholls.com/Electronics_Resources/QuestionIndex.html

© Paul Nicholls

August 2020



Electronics Resources by Paul Nicholls is licensed under a [Creative Commons Attribution 4.0 International License](https://creativecommons.org/licenses/by/4.0/).