
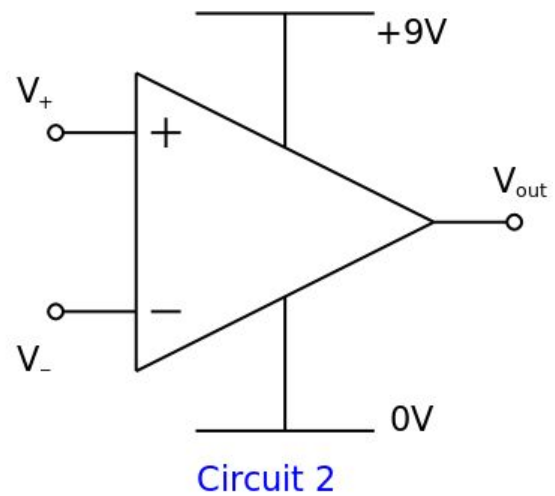


Comparator Exercises

Question 1

Consider the circuits shown below:

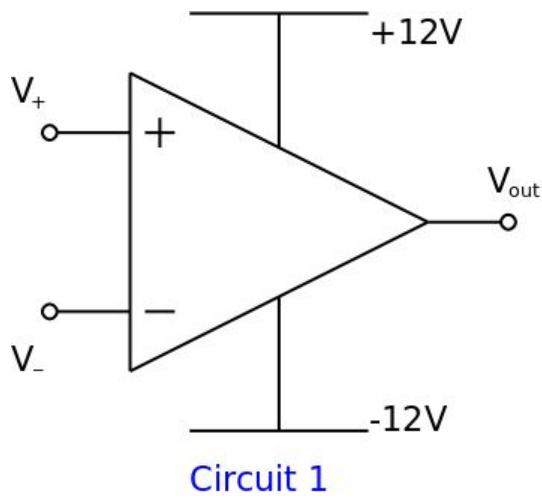

What is the value of V_{out} when:


- A. $V_+ = +2V$ and $V_- = +3V$ in circuit 1?
- B. $V_+ = +3V$ and $V_- = +2V$ in circuit 1?
- C. $V_+ = -2V$ and $V_- = +3V$ in circuit 1?
- D. $V_+ = -2V$ and $V_- = -3V$ in circuit 1?
- E. $V_+ = +4V$ and $V_- = +5V$ in circuit 2?
- F. $V_+ = +5V$ and $V_- = +3V$ in circuit 2?
- G. $V_+ = +6V$ and $V_- = +3V$ in circuit 2?
- H. $V_+ = +3V$ and $V_- = +6V$ in circuit 2?
- I. $V_+ = +2V$ and $V_- = +2V$ in circuit 1?
- J. $V_+ = -2V$ and $V_- = -2V$ in circuit 1?
- K. $V_+ = 0V$ and $V_- = 0V$ in circuit 1?

Question 2

Consider the comparator circuits shown below.

When the light intensity is **600 Lux**, the resistance of the LDR is **4 k Ω** .

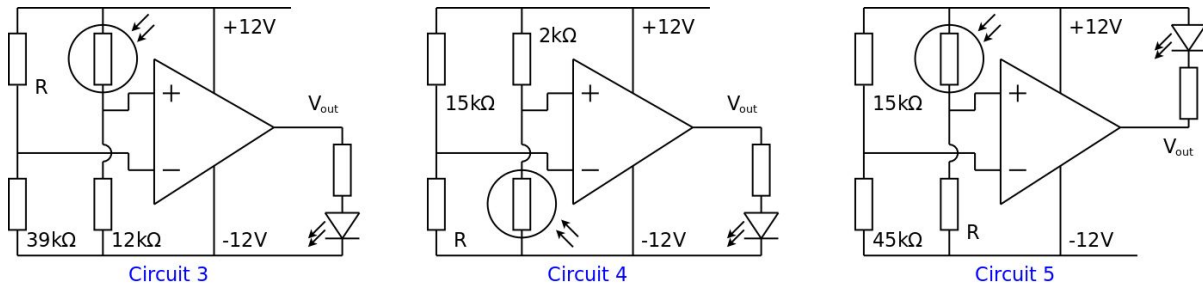In each circuit the LED changes state (goes from ON to being OFF or from OFF to being ON) when the light level is 600 Lux.



- A. In circuit 3, what is the state of the LED when the light level is 800 Lux?
- B. In circuit 3, what is the value of the resistor labelled R?

- C. In circuit 4, what is the state of the LED when the light level is 800 Lux?
- D. In circuit 4, what is the value of the resistor labelled R?

- E. In circuit 5, what is the state of the LED when the light level is 800 Lux?
- F. In circuit 5, what is the value of the resistor labelled R?

Comparator Exercises Answers

Question 1

- A. -10V It should be -12V but V_{out} is always 2V away from the power supply
- B. +10V
- C. -10V -2 < +3
- D. +10V -2 > -3
- E. +2V It should be 0V but V_{out} is always 2V away from the power supply
- F. +7V
- G. +7V
- H. +2V
- I. 0V There is no difference between the inputs
- J. 0V
- K. 0V

Question 2

- A. ON Light intensity is greater, resistance of the LDR is less, V_+ is higher
- B. 13k Ω AT 600 Lux, 4k Ω : 12k Ω = R : 39k Ω , R = 13k Ω (ratio 1:3)
- C. OFF
- D. 30k Ω
- E. OFF As for question A., V_+ is higher, V_{out} = +10V, the LED is OFF
- F. 12k Ω