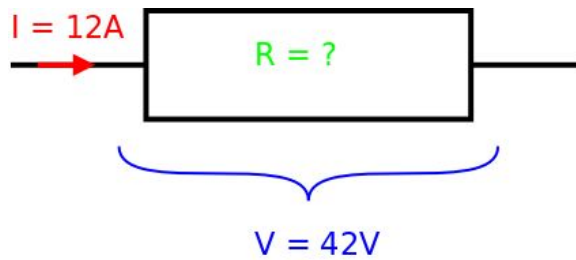


Resistance Exercises


Question 1



A current of 12 amps flows through a resistor. The potential difference across the resistor is 42 volts.

What is the value of the resistor?


Question 2

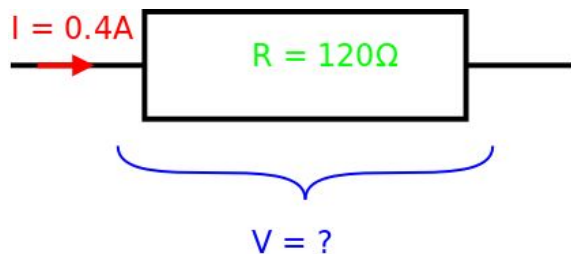

A current of 0.4 A flows through a $120\ \Omega$ resistor.

What is the potential difference across the resistor?

Question 3

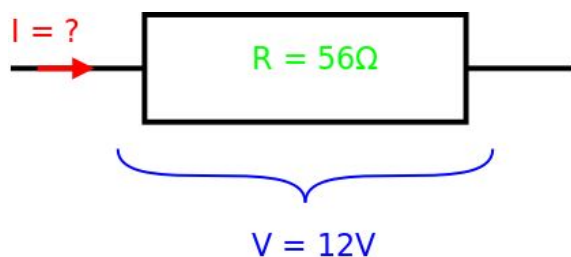

There is a potential difference of 12 V across a $56\ \Omega$ resistor.

What current flows through the resistor?

Question 4

A current of 4 mA flows through a $12\ \text{k}\Omega$ resistor.

What is the potential difference across the resistor?

Question 5

A current of 200 mA flows through a resistor when there is a potential difference of 10 V across the resistor.


What is the value of the resistor?

Question 6

A student uses a voltmeter to measure the potential difference across a $220\ \Omega$ resistor. The reading on the voltmeter is 4.2 V.

What current is flowing through the resistor?

Question 7

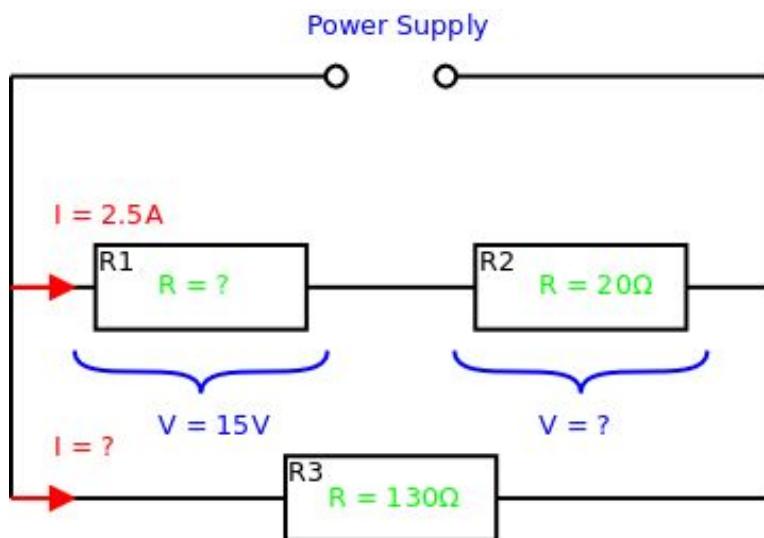

For the circuit shown:

- What is the value of the resistor R1?
- What is the potential difference across resistor R2?
- What is the current through resistor R3?
- What is the EMF of the power supply?

Answers

Question 1

$$R = V / I \text{ therefore } R = 42 / 12 = 3.5 \Omega$$

Question 2

$$V = I \times R \text{ therefore } V = 0.4 \times 120 = 48 \text{ V}$$

Question 3

$$I = V / R \text{ therefore } I = 12 / 56 = 0.21 \text{ A} \quad \text{Note: Only 2 sig fig. Not } I = 0.214 \text{ A}$$

Question 4

$$V = I \times R, 4 \text{ mA} = 4 \times 10^{-3} \text{ A} \text{ and } 12 \text{ k}\Omega = 12 \times 10^3 \Omega \text{ therefore } V = 4 \times 10^{-3} \times 12 \times 10^3 = 48 \text{ V}$$

Question 5

$$R = V / I, 200 \text{ mA} = 0.2 \text{ A} \text{ therefore } R = 10 / 0.2 = 50 \Omega$$

Question 6

$$I = V / R \text{ therefore } I = 4.2 / 220 = 0.019 \text{ A} \text{ or } I = 19 \text{ mA} \quad \text{Note: Answer is to 2 sig. Fig.}$$

Question 7

a) $R = V / I$ therefore $R = 15 / 2.5 = 6 \Omega$

b) $V = I \times R$ and $I = 2.5 \text{ A}$ because R_1 and R_2 are in series. $V = 2.5 \times 20 = 50 \text{ V}$

c) $I = V / R$ and $V = 65 \text{ V}$ because R_3 is in parallel with R_1 and R_2 . $I = 65 / 130 = 0.5 \text{ A}$

d) The EMF of the power supply is 65 V because it is in parallel with R_3