

Timing Circuits Exercises

Question 1

Calculate the time constant of an RC circuit where $C = 100\ \mu\text{F}$ and $R = 47\ \text{k}\Omega$

Question 2

An RC circuit has a time constant of 100 ms and a capacitor value of $C = 56\ \text{nF}$. Calculate the value of the resistor in the circuit

Question 3

Calculate the time period of a 555 monostable where the timing component are $C = 220\ \mu\text{F}$ and $R = 120\ \text{k}\Omega$

Question 4

A NAND gate monostable requires a time period of 20 ms and uses a resistor value of $1\ \text{M}\Omega$. Calculate a suitable value for the timing capacitor

Question 5

Give one advantage of using a NAND gate monostable instead of a 555 monostable

Question 6

A 555 monostable requires a time period of 1.0 s with a capacitor value of $47\ \mu\text{F}$. Calculate a suitable resistor value

Question 7

A 555 astable uses a $10\ \text{k}\Omega$ resistor for R_a , a $22\ \text{k}\Omega$ for R_b and $C = 33\ \mu\text{F}$. Calculate the time period of the astable circuit

Question 8

For the astable in question 7, calculate the frequency of the astable circuit

Question 9

For the astable in question 7, calculate the mark-space ratio

Timing Circuits Answers

Question 1

Using $\tau = RC$ gives the time constant as $\tau = 47 \times 10^3 \times 100 \times 10^{-6} = 4.7 \text{ s}$

Question 2

Rearranging $\tau = RC$ gives $R = \tau / C$ therefore $R = 100 \times 10^{-3} / 56 \times 10^{-9} = 1.8 \text{ M}\Omega$

Question 3

Using $T = 1.1RC$ gives a time period of $T = 1.1 \times 120 \times 10^3 \times 220 \times 10^{-6} = 29 \text{ s}$

Question 4

$T = 0.7RC$ gives $C = T / (0.7R)$ therefore $C = 20 \times 10^{-3} / (0.7 \times 1 \times 10^6) = 29 \text{ nF}$

Question 5

A NAND gate monostable will give the required time period even when the trigger is held permanently LOW.

Question 6

Rearranging $T = 1.1RC$ gives $R = T / (1.1C)$. $R = 1 / (1.1 \times 47 \times 10^{-6}) = 19 \text{ k}\Omega$

Question 7

Using $T = 0.7(R_a + 2R_b)C$ gives $T = 0.7 \times (10 \times 10^3 + 2 \times 22 \times 10^3) \times 33 \times 10^{-6} = 1.2 \text{ s}$

Question 8

Using $f = 1 / T$ gives $f = 1 / 1.2 = 0.8 \text{ Hz}$

Question 9

Using the equation for mark-space ratio, $T_{\text{ON}} / T_{\text{OFF}} = (R_a + R_b) / R_b$, the mark-space ratio is given by $(10 + 22) / 22 = 1.45$. The mark-space ratio is 1.45:1.0